

# Unit 3.3: Using Laplace Transforms for Circuit Analysis

## Contents

- [Colophon](#)
- [Agenda](#)
- [Circuit Transformation from Time to Complex Frequency](#)
- [Complex Impedance  \$Z\(s\)\$](#)
- [Complex Admittance  \$Y\(s\)\$](#)
- [Reference](#)

The preparatory reading for this section is [Chapter 4 \[Karris, 2012\]](#) which presents examples of the applications of the Laplace transform for electrical solving circuit problems.

## Colophon

An annotatable worksheet for this presentation is available as [Worksheet 6](#).

- The source code for this page is [laplace\\_transform/3/circuit\\_analysis.ipynb](#).
- You can view the notes for this presentation as a webpage ([HTML](#)).
- This page is downloadable as a [PDF](#) file.


## Agenda

We look at applications of the Laplace Transform for


- Circuit transformation from Time to Complex Frequency
- Complex impedance
- Complex admittance

## Circuit Transformation from Time to Complex Frequency
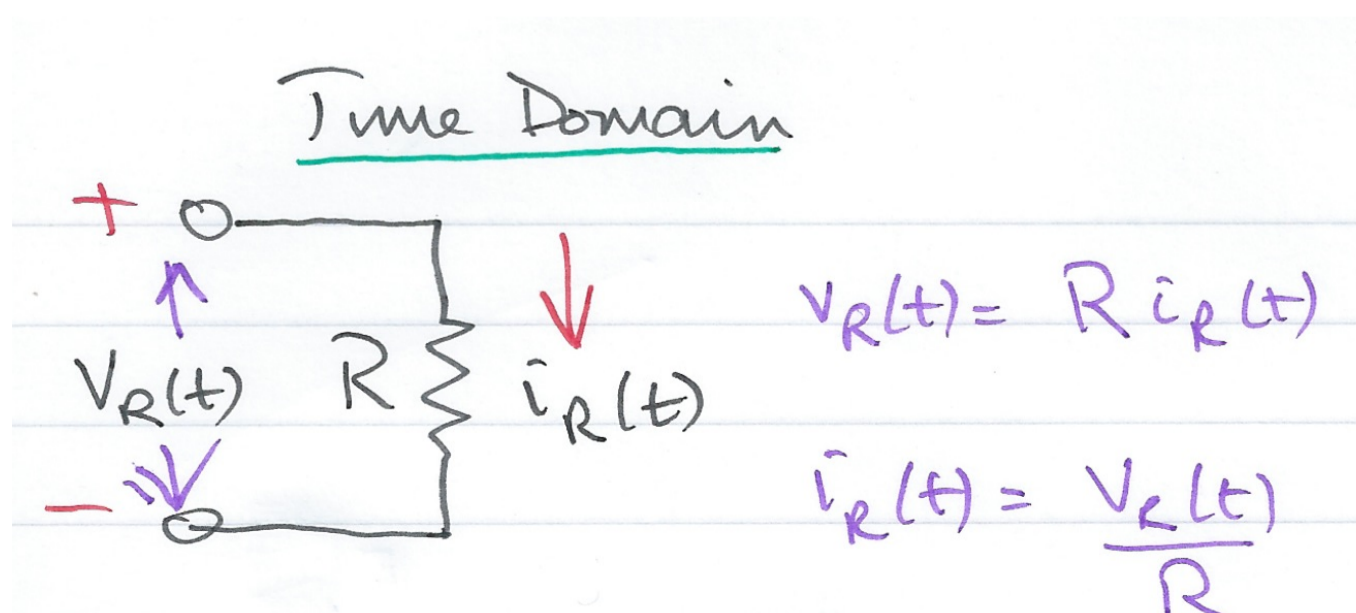
### Time Domain Model of a Resistive Network




## Complex Frequency Domain Model of a Resistive Circuit

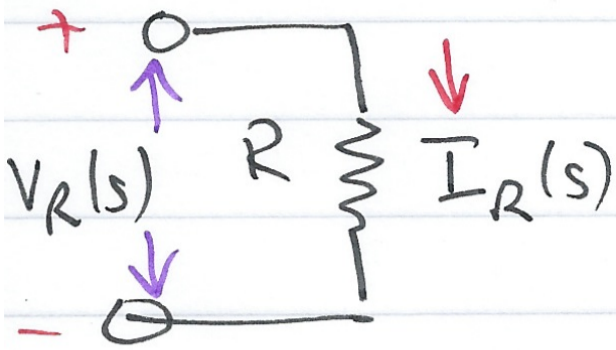Frequency Domain

$$V_R(s) = R I_R(s)$$

$$I_R(s) = \frac{V_R(s)}{R}$$


## Time Domain Model of an Inductive Network

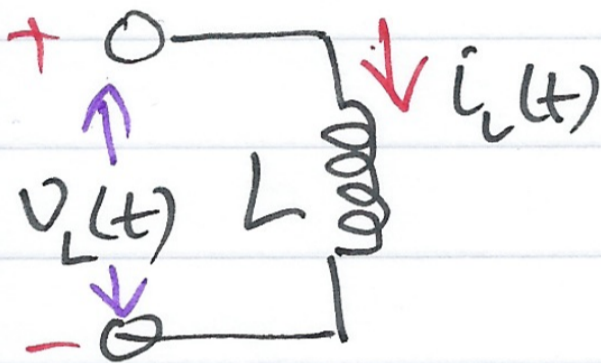Time Domain

$$V_L(t) = L \frac{di_L}{dt}$$

$$i_L(t) = \frac{1}{L} \int_{-\infty}^t v_L dt$$


## Complex Frequency Domain Model of an Inductive Network

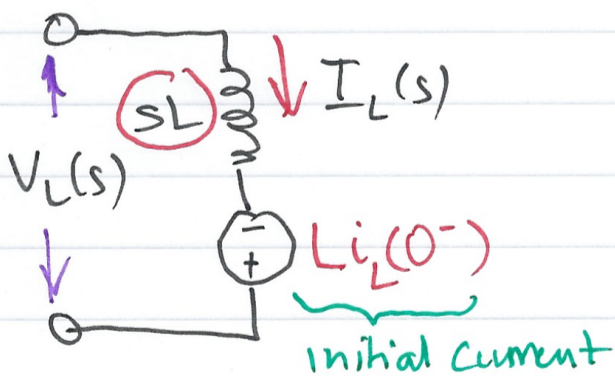Frequency Domain

$$V_L(s) = sL I_L(s) - Li_L(0^-)$$

$$I_L(s) = \frac{V_L(s)}{Ls} + \frac{Li_L(0^-)}{s}$$


## Time Domain Model of a Capacitive Network

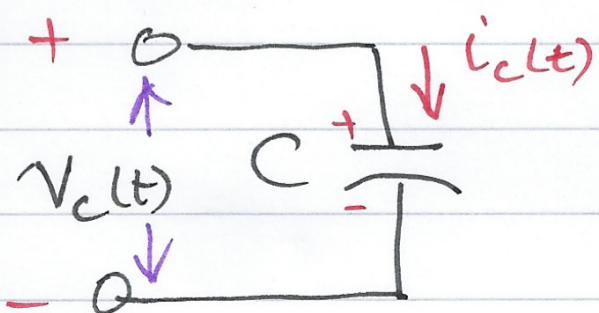Time Domain

$$i_C(t) = C \frac{dv_C}{dt}$$

$$v_C(t) = \frac{1}{C} \int_{-\infty}^t i_C dt$$
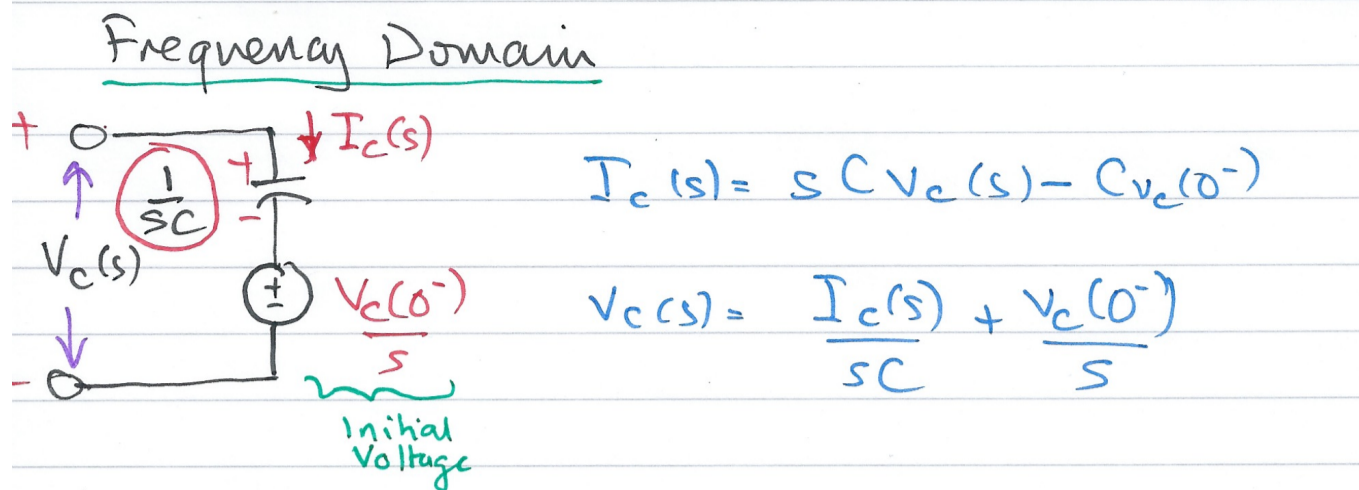
## Complex Frequency Domain of a Capacitive Network




### Examples

We will work through these in class. See [worksheet 6](#).
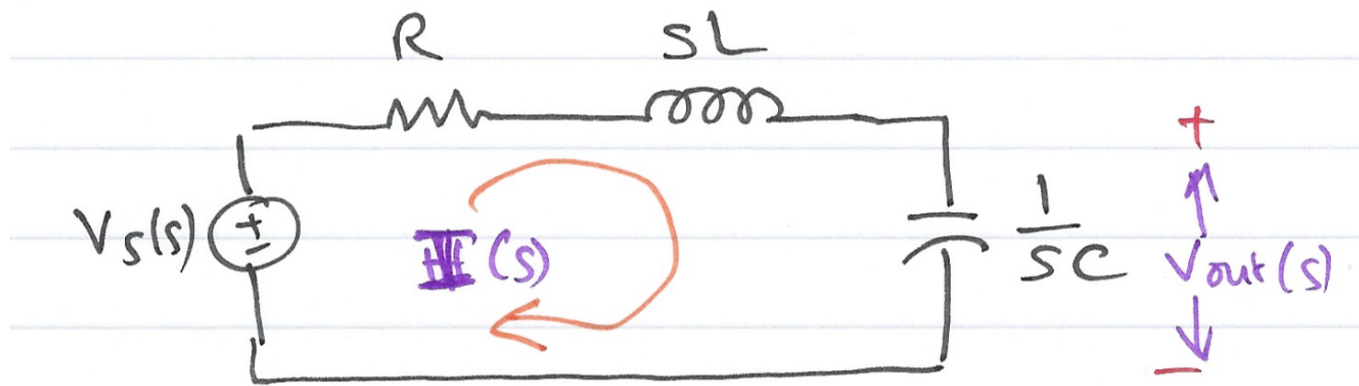
## Complex Impedance $Z(s)$

Consider the  $s$ -domain RLC series circuit, where the initial conditions are assumed to be zero.



For this circuit, the sum

$$R + sL + \frac{1}{sC}$$

represents that total opposition to current flow. Then,

$$I(s) = \frac{V_s(s)}{R + sL + 1/(sC)}$$

and defining the ratio  $V_s(s)/I(s)$  as  $Z(s)$ , we obtain

$$Z(s) = \frac{V_s(s)}{I(s)} = R + sL + \frac{1}{sC}$$

The  $s$ -domain current  $I(s)$  can be found from

$$I(s) = \frac{V_s(s)}{Z(s)}$$


where

$$Z(s) = R + sL + \frac{1}{sC}.$$

Since  $s = \sigma + j\omega$  is a complex number,  $Z(s)$  is also complex and is known as the *complex input impedance* of this RLC series circuit.
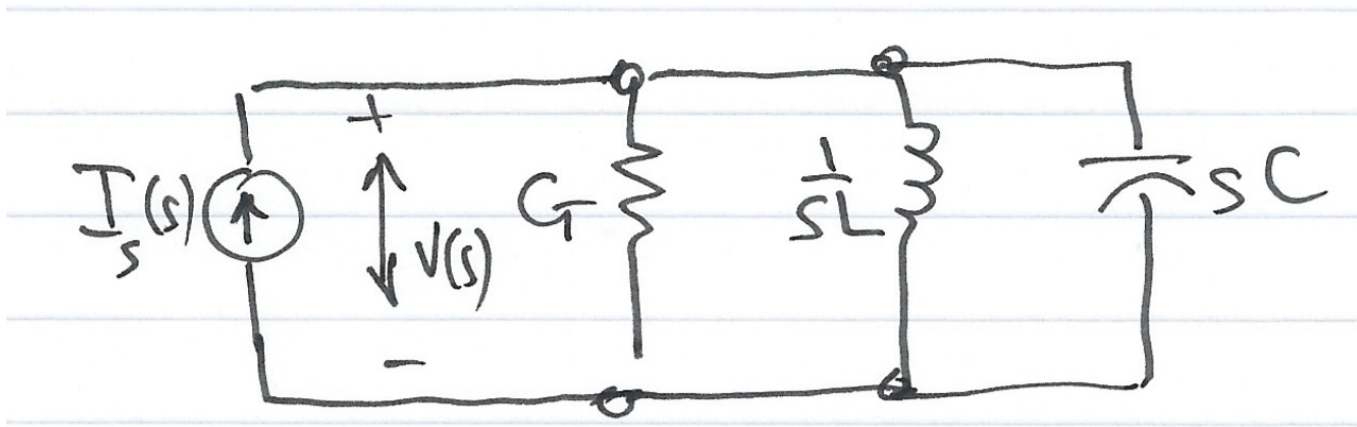
## Complex Admittance $Y(s)$

Consider the  $s$ -domain GLC parallel circuit shown below where the initial conditions are zero.



For this circuit

$$GV(s) + \frac{1}{sL}V(s) + sCV(s) = I_s(s)$$

$$\left(G + \frac{1}{sL} + sC\right)V(s) = I_s(s)$$

Defining the ratio  $I_s(s)/V(s)$  as  $Y(s)$  we obtain

$$Y(s) = \frac{I_s(s)}{V(s)} = G + \frac{1}{sL} + sC = \frac{1}{Z(s)}$$

The  $s$ -domain voltage  $V(s)$  can be found from

$$V(s) = \frac{I_s(s)}{Y(s)}$$

where

$$Y(s) = G + \frac{1}{sL} + sC.$$

$Y(s)$  is complex and is known as the *complex input admittance* of this GLC parallel circuit.

## Reference

See [Bibliography](#).

By Dr Chris P. Jobling

© Copyright Swansea University (2019-2022).

This page was created by [Dr Chris P. Jobling](#) for [Swansea University](#).